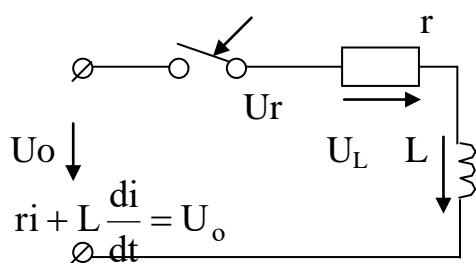


24-ma`ruza. Oddiy elektr zanjirlarida o`tkinchi jarayonlarni klassik usulda xisoblash.

Reja

- 1.O`tkinchi jarayonni qisoblashning klassik usuli.
- 2.Kondensatorning aperiodik, chegaraviy aperiodik va tebranma zaryadsizlanishi.

r,l elementlari ketma-ket ulangan zanjirni o`zgarmas kuchlanish manbaiga ulash.



Zanjir t=0 da o`zgarmas kuchlanish U_o ga ulanadi
Zanjirning differensial tenglamasi:

—

Unga mos bir jinsli tenglama quyidagi ko`rinishga ega:

$$L \frac{di_{\text{opk}}}{dt} + ri_{\text{opk}} = 0$$

i_{opk} aniqlaymiz, uning xarakteristik tenglamasi quyidagicha bo`ladi:

$$L\alpha + r = 0$$

$$U \text{ birgina xaqiqiy va manfiy } \alpha = -\frac{r}{L}$$

$$i_{\text{opk}} = Ae^{\alpha t} = Ae^{-\frac{r}{L}t} = Ae^{-\frac{t}{\tau}}$$

$$\text{bunda: } \alpha = -\frac{r}{L} \quad \text{so`nish koeffisienti}$$

Integrallash doimiysini A boshlang`ich shartlar orqali aniqlaymiz. Kommutatsiyaga qadar zanjirdan tok o`tmagan:


$$i_-(0) = 0$$

demak zanjirni ularash paytida xam u nolga teng bo`lgan $i(0) = 0$ Zanjirda o`tkinchi protsess tugagandan so`ng, faqat r ning qarshiligi bilan aniqlanadigan $i_{\text{typr}} = \frac{U_0}{r}$ tok bo`ladi, unda:

$$i(0) = i_{\text{typr}}(0) + i_{\text{epk}}(0) = \frac{U_0}{r} + A = 0$$

Shunday qilib $A = -\frac{U_0}{r}$ A bo`lib o`tkinchi tok i esa:
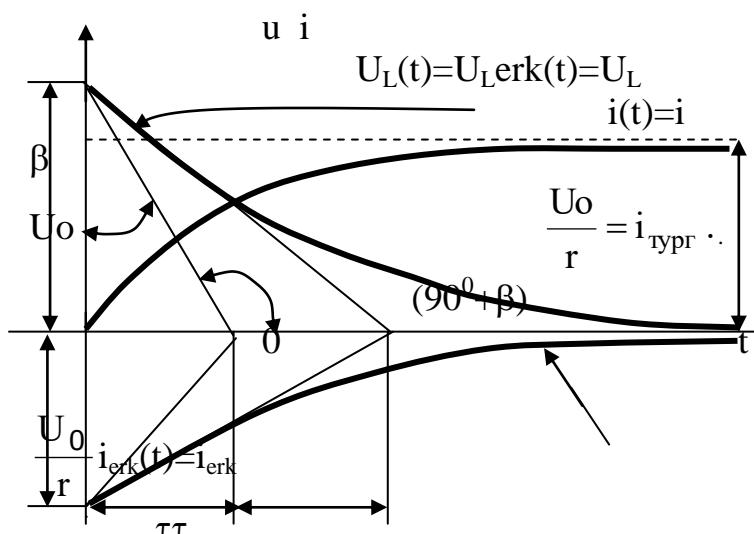
$$i = i_{\text{typr}} + i_{\text{epk}} = \frac{U_0}{r} - \frac{U_0}{r} e^{-\frac{t}{\tau}} = \frac{U_0}{r} (1 - e^{-\frac{t}{\tau}})$$



τ -vaqt doimiysi; $\tau = L/r$.

Zanjirning ayram elementlaridagi o`tkinchi kuchlanishlarni aniqlash mumkin:

$$U_r = ri = U_o (1 - e^{-\frac{t}{\tau}})$$

$$U_L = L \frac{di}{dt} = \frac{L}{r} U_o \left[0 - \left(-\frac{1}{\tau} \right) e^{-\frac{t}{\tau}} \right] = U_o e^{-\frac{t}{\tau}}$$


Masala:

Berilgan: $r=50 \text{ Om}$, $L=0,1 \text{ Gn}$, $U_o=200 \text{ B}$.

$$\tau = \frac{L}{r} = 0,002 \text{ cek}; \quad i_{\text{turg}} = I_0 = \frac{U_0}{r} = \frac{200}{50} = 4 \text{ A}; \quad t = 5\tau = 0,01 \text{ cek.}$$

$$i = I_0 (1 - e^{-\frac{t}{\tau}}) = 4 (1 - e^{-5}) = 4 \cdot 0,099325 = 3,97 \text{ A}$$

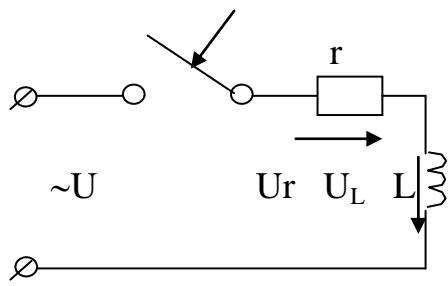R,l elementlari ketma-ket biriktirilgan zanjirni sinusoidal o`zgaruvchan kuchlanish manbaiga ularash.



r va L sinusoidal kuch $U=Um \sin(\omega t + \psi_e)$

$$L \frac{di}{dt} + ri = U_m \sin(\omega t + \psi_u) \text{ bo`lib}$$

turg`unlashgan tok:

$$i_{typr} = \frac{U_m}{Z} \sin(\omega t + \psi_u - \varphi) \text{ ni xosil qiladi.}$$

bu yerda: $Z = \sqrt{r^2 + \omega^2 L^2}$ – zanjirning to`la qarshiligi

$\varphi = \operatorname{arctg} \frac{\omega L}{r}$ – kuchlanish u va tok i_{turg} orasidagi siltish burchagi.

Oldingi paragrafdan ma'lumki, tok=erkin tashkil etib:

$$i_{\varphi pk} = A e^{-\frac{t}{\tau}}$$

Bunda zanjirdagi o`tkinchi tok qo`yidagicha o`zgaradi:

$$i = i_{typr} + i_{\varphi pk} = \frac{U_m}{Z} \sin(\omega t + \psi_u - \varphi) + A e^{-\frac{t}{\tau}}$$

A-ni aniqlash uchun boshlang`ich shartlarga murojat qilamiz, kommutatsiya birinchi qonuniga ko`ra:

$$i(0) = (0) = \frac{U_m}{Z} \sin(\psi_u - \varphi) + A = 0 \text{ ga egamiz}$$

$$\text{bundan: } A = -\frac{U_m}{Z} \sin(\psi_u - \varphi)$$

$$i = \frac{U_m}{Z} \sin(\omega t + \psi_u - \varphi) - \frac{U_m}{Z} \sin(\psi_u - \varphi) e^{-\frac{t}{\tau}} \text{ bo`ladi.} \quad (1)$$

Induktivlik g`altagining qismalaridagi o`tkinchi kuchlanish qo`yidagicha:

$$U_L = L \frac{di}{dt} = \frac{\omega L}{Z} U_m \cos(\omega t + \psi_u - \varphi + \frac{\pi}{2}) + \frac{r}{Z} U_m \sin(\psi_u - \varphi) e^{-\frac{t}{\tau}} =$$

(2)

$$= U_m \left[\sin \varphi \cos(\omega t + \psi_u - \varphi + \frac{\pi}{2}) + \cos \varphi \sin(\psi_u - \varphi) e^{-\frac{t}{\tau}} \right]$$

Induktivlikdagi o`tkinchi tok va kuchlanish uchun olingan ifodalarning to`g`riligiga vakt t ga 0 dan ∞ gacha chegaraviy qiymatlar berib ishonch qosil qilish mumkin. Masalan, vaqt t=0 da (1) ning o`ng qismi nolga aylanadi, bu esa induktivlikdagi tok uchun kommutatsiya qonuni tasdiqlaydi:

$$i_-(0) = i(0) = 0$$


O`tkinchi protsess tugagandan so`ng t= ∞ da:

$$i = i_{typ} = \frac{U_m}{Z} \sin(\omega t + \psi_u - \varphi)$$

chunki $i_{erk}=0$ 2- tenglamaga ko`ra kommutatsiya paytida:


$U_L(0) = U_m [\sin \varphi \cos(\psi_u - \varphi) + \cos \varphi \sin(\psi_u - \varphi)] = U_m \sin \psi$
bo`ladi, ya’ni t=0 g`altak qismlardagi kuchlanish zanjirga berilgan kuchlanishning oniy qiymatiga teng.

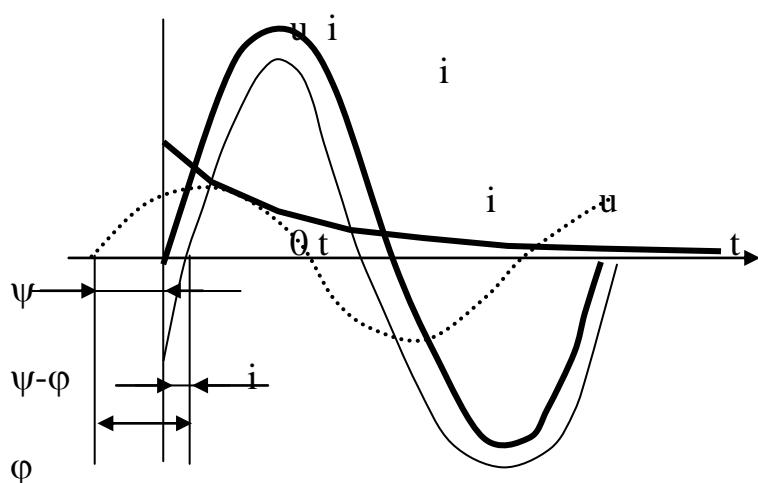O`tkinchi tok va o`tkinchi kuchlanish egri chiziqlari



a)

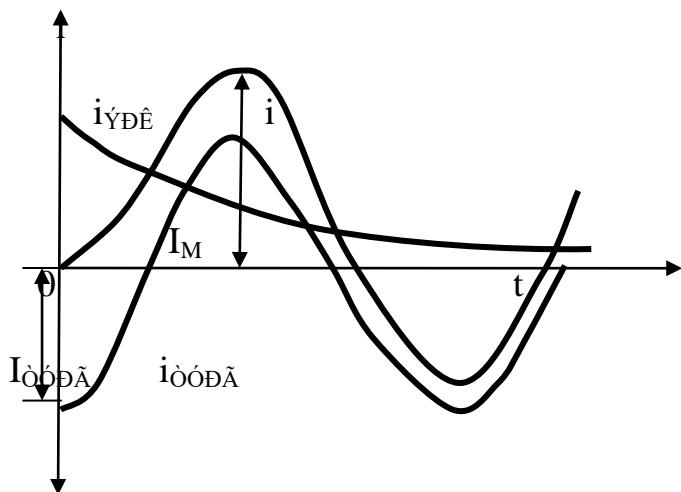- a) rasmda $\psi > 0$, $\varphi > 0$ va $\psi - \varphi < 0$ xollar uchun zanjirga berish kuchlanish $u = U_m \sin(\omega t + \varphi)$ ning(punktir chiziq) va o`tkinchi tok i ning(yo`g`on chiziq) egri chiziq ko`rsatilgan $i_{epk} = -\frac{U_m}{Z} \sin(\psi_u - \varphi) e^{-\frac{t}{\tau}}$ mikdori va yo`nalish kommutatsiya paytida i_{turg} ning boshlang`ich fazasiga bog`liq $\psi_i = \psi_u - \varphi$.



á)

Agar kuchlanishéiňa fazasi ψ_U siltish burchagi φ ga teng bo`lib qolsa, u xolda o`tkinchi tok i faqat turg`un tok i_{TURG} ning qiymatidan iborat bo`ladi, chunki 1-tenglamaga asosan $i_{ERK} = 0$ bo`ladi. Shunda zanjir ulanganda tebranishsiz sinusoidal tok $i = \frac{U_m}{Z} \sin\omega t$ turg`unlashadi. Agar zanjirni ularash $\psi = \varphi \pm \frac{\pi}{2}$ da sodir bo`lsa, erkin tokning boshlang`ich chayqalishi o`zining maksimum qiymatiga erishadi $i_{opk}(0) = \pm \frac{U_m}{Z}$ (b-rasm).

Shu tufayli zanjirga berilgan kuchlanish davrining yarimiga teng bo`lgan vaqt dan so`ng, o`tkinchi tok xam o`zining eng katta qiymati i_{max} -ga erishadi. Ammo nazariy jixatdan tokning bu maksimumi xatto vaqt doimiysi τ ning eng katta qiymatlarida xam turg`unlashgan tok amplitudaviy qiymatining ikkilanganidan ortmaydi.

R,L elementlari ketma-ket ulangan zanjirda qisqa tutashuv.

Boshlang`ich toki $i(0) \neq 0$ noldan farq qiladigan r , L elementi ketma-ket ulangan zanjir qisqa tutashganda vujudga keluvchi o`tkinchi protsesslarni ko`ramiz. Zanjir kommutatsiyaga qadar qo`shimcha rezistor r_o orqali o`zgarmas kuchlanish U_o ga ulangan $t=0$ da qisqa tutashadi deb faraz qilamiz. Kommutatsiyaga qadar turg`un tok:

$$I_0 = \frac{U_o}{r_o + r} \text{ bo`lsa,}$$

kommutatsiyadan so`ng nolga teng, chunki kontur manbadan ajratilgan bo`lib, ilgari g`altakka tok I_0 olib kirgan magnit maydonning energiyasi

$$W_m = \frac{LI_0^2}{2}$$

rezistor r da issiqlik energiyasiga aylanib, asta sekin nolgacha kamayadi. O`tkinchi rejimdagи zanjirning differensial tenglamasi:

$$L \frac{di_{\text{opk}}}{dt} + ri_{\text{opk}} = 0$$

bo`ladi, o`tkinchi tok esa: $i = i_{\text{opk}} = Ae^{-\frac{t}{\tau}}$

Integrallash doimiysi Ani $i_{-(0)} = i(0)$ shartidan topamiz, ya'ni $\frac{U_0}{r_0 + r} = A$

$$\text{Shunday qilib: } i = \frac{U_0}{r_0 + r} e^{-\frac{t}{\tau}} = I_0 e^{-\frac{t}{\tau}}$$

Induktiv g`altakdagi o`tkinchi kuchlanish:

$$U_L = L \frac{di}{dt} = -\frac{U_0 r}{r_0 + r} e^{-\frac{t}{\tau}} = -rI_0 e^{-\frac{t}{\tau}}$$

Ya'ni rezistordagi kuchlanish tushuvi:


$$U_r = ri = rI_0 e^{-\frac{t}{\tau}}$$

ga teng bo`lib ishorasi qarama-qarshi kommutatsiya paytida o`tkinchi tokning avvalgi qiymati:

$$i_{-(0)} = i(0) = I_0$$

ni saqlagan tok i dan farqli induktiv g`altakdagi kuchlanishi $u_{L-}(0)=0$ dan $U_L(0) = -rI_0$ gacha sakrab o`tishi mumkin(b-chizma).

G`altakdagi e.yu.k. $e_L = -L \frac{di}{dt}$ ning qo`yib ishoralari kuchlanishga va tokning vaqt bo`yicha o`zgarishga bog`liq. Agar induktiv tarmoqdagi tok orta borsa e.yu.k. ning ishorasi $e_L = -u_L$ manfiy, kamaya borsa musbat bo`ladi. Shunday qilib induktiv g`altakni o`zgarmas kuchlanishni manbai ulash va ajratish tokning qar qanday o`zgarishi e.yu.k. xosil qilishga va uning zanjirdagi boshlangich muvozanat xolatini saqlab turishiga sabab bo`ladi.

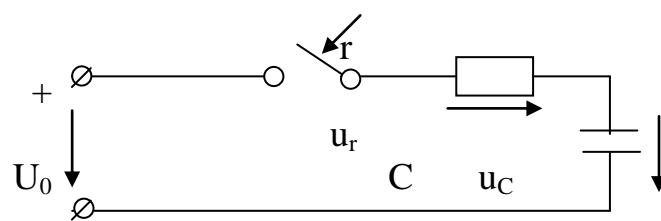

Chizmada vaqtning $t=0$ paytida r, C elementlari ketma-ket ulangan zanjirni o'zgarmas kuchlanish U_0 manbaiga ulash sxemasi ko`rsatilgan. Sig`imdag'i kuchlanish U_C ni o'zgaruvchan xisoblab zanjirning differensial tengëàìàñèiè tuzamiz:

$$rC \frac{dU_C}{dt} + U_C = U_0$$

bunda: $i=i=\frac{dq}{dt}=C\frac{dU_C}{dt}$ kondensator S qoplamalaridagi o'tkincha tok.

Sig`imdag'i o'tkinchi kuchlanish $U_C=U_{turg}+U_{erk}$

$$rC \frac{dU_{C_{epk}}}{dt} + U_{C_{epk}} = 0$$

Bunga mos xarakteristik tenglama:

$$rC\alpha + 1 = 0$$

dan chastota o'lchash $\frac{1}{cek}$, $\alpha = -\frac{1}{rC}$ ni topamiz.

So'nish koeffisienti α -ning ishorasiga ko'rà,

$$U_{C_{epk}} = Ae^{\alpha t} = Ae^{-\frac{t}{rC}}$$

Integrallash doimiysi A ni boshlangich shartlardan topamiz:


$$\begin{aligned} U_C(0) &= U_C(0) \\ U_C(0) &= 0 = U_{C_{typ}}(0) + U_{C_{epk}}(0) = U_0 + A \\ &\text{yoki} \\ A &= -U_0 \end{aligned}$$

Kommutatsiyaga qadar sig`imdag'i kuchlanish nolga teng $U_C(0)=0$. O'tkinchi protsess tugagandagi turg'unlashgan kuchlanish $U_{Sturg}=U_0$, chunki o'zgarmas tokda kondensatorning qarshiligi ∞ (tok o'tmaydi) zanjirdagi tok $i_{turg}=0$.

Sig`imdag'i kuchlanish:

$$U_C = U_{C_{typ}} + U_{C_{epk}} = U_0 - U_0 e^{-\frac{t}{\tau}} = U_0 (1 - e^{-\frac{t}{\tau}})$$

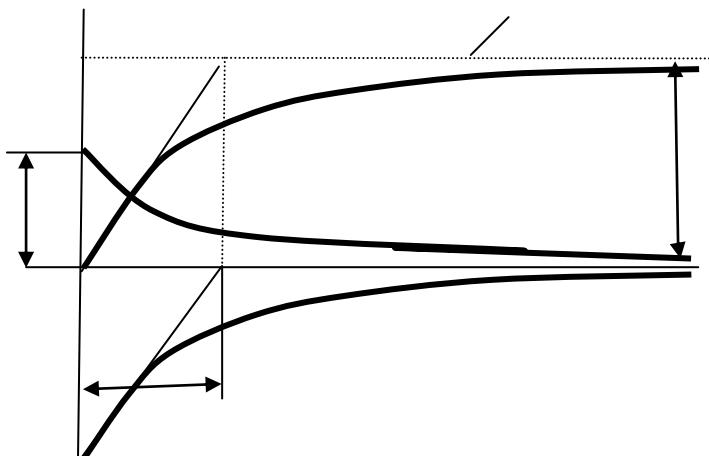
$\tau=rC$ –o'tkinchi protsessning intensivligini xarakterlovchi vaqt doimiysi (sek), u qanchalik katta bo`lsa S ning zaryadlanishi shunchalik sekin boradi va aksincha.



$$O'tkinchi tok i = C \frac{dU_C}{dt} \quad binoan:$$

$$i = CU_0 \left[0 - \left(-\frac{1}{rC} e^{-\frac{t}{\tau}} \right) \right] = \frac{U_0}{r} e^{-\frac{t}{\tau}}$$

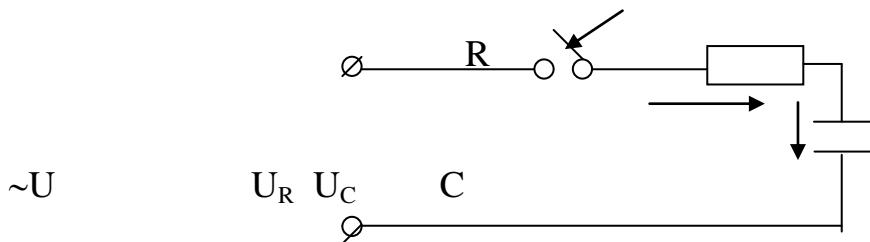R,c elementlari ketma-ket ulangan zanjirni sinusoidal o'zgaruvchan kuchlanish manbaiga ularash.



r C elementlar ketma-ket ulangan zanjir $U = U_m \sin(\omega t + \varphi_u)$ manbaga ularanda o'tkincha kuchlanish va toklar o'zgarish qoqunlarini aniqlaymiz.
O'tkinchi kuchlanish:

$$U_C = U_{C_{typ}} + U_{C_{epk}}$$

Bularning birinchisi i_{turg} ñà bog'liq ikkinchisi esa $u_{C_{epk}} = Ae^{-\frac{t}{\tau}}$ ñà òáíá.

$$i_{typ} = \frac{U_m}{Z} \sin(\omega t + \psi_u - \varphi) bo'ladi$$

áunda: $Z = \sqrt{r^2 + \left(\frac{1}{\omega C}\right)^2}$ – zanjiriéíä to'la qarshiligi,

$\varphi = \arctg \left(-\frac{1}{r\omega C} \right)$ – o'tkinchi protsess tugagandan keyingi u ñà i orasidagi siljish burchagi.

$$U_{C_{\text{ty pr}}} = \frac{U_m}{z\omega C} \sin(\omega t + \psi_u - \varphi - \frac{\pi}{2})$$

chunki u tokdan $\frac{\pi}{2}$ burchakka orqada qoladi, unda:

$$U_C = \frac{U_m}{z\omega C} \sin(\omega t + \psi_u - \varphi - \frac{\pi}{2}) + A e^{-\frac{t}{\tau}}, \quad \tau = rC$$

Integrallash doimiysi A ni boshlangich shartlardan aniqlanadi:

$$U_C(0) = 0 = \frac{U_m}{z\omega C} \sin(\psi_u - \varphi - \frac{\pi}{2}) + A$$


$$\text{bu yerdan: } A = -\frac{U_m}{z\omega C} \sin(\psi_u - \varphi - \frac{\pi}{2})$$

U_S -kuchlanishning o`zgarish qonuni quyidagicha:

$$U_C = \frac{U_m}{z\omega C} \sin(\omega t + \psi_u - \varphi - \frac{\pi}{2}) - \frac{U_m}{z\omega C} \sin(\psi_u - \varphi - \frac{\pi}{2}) e^{-\frac{t}{\tau}}$$

Bundan o`tkinchi tok $i = C \frac{dU_c}{dt}$ ni topamiz:
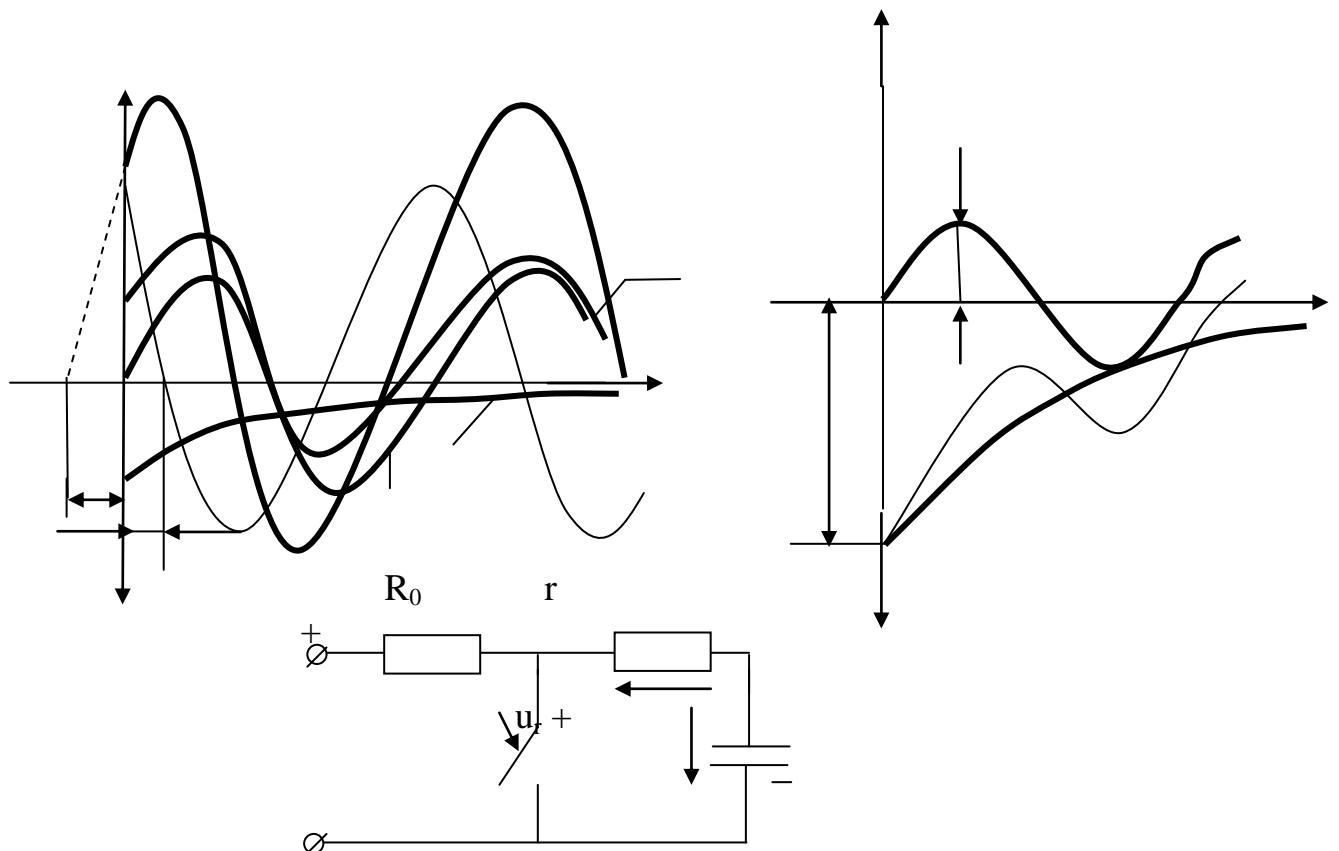
$$i = \frac{U_m}{z} \sin(\omega t + \psi_u - \varphi) + \frac{U_m}{z} \frac{1}{r\omega C} \sin(\psi_u - \varphi - \frac{\pi}{2}) e^{-\frac{t}{rC}}$$




$$u_0 \quad C$$

$$U_C = U_{C0} e^{-\frac{t}{\tau}} \quad \tau = RC$$

Integrallash doimiysi boshlang`ich shartlar yordamida aniqlanadi:

$$\begin{aligned} u_C(0) &= u_C(0) = u_0 \\ u_C(0) &= A = u_0 \text{ bo`ladi yoki} \\ u_C &= u_0 e^{-\frac{t}{\tau}} \end{aligned}$$

Zanjirdagi o`tkinchi tok:

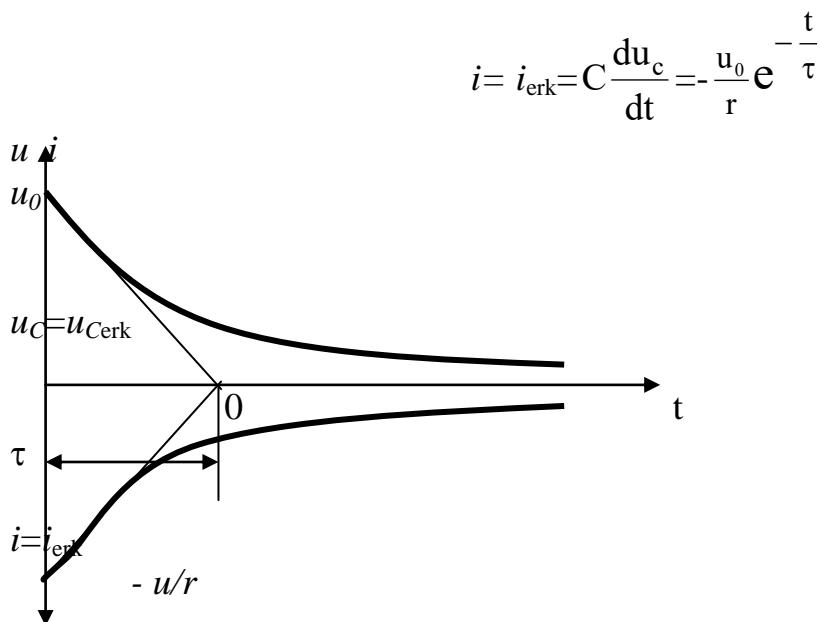


O`tkinchijarayon ($t=0$ dant= ∞ gacha) davomidaqarshilik R

$$W_r = \int_0^\infty i^2 R dt = -\frac{u_0^2}{r} \int_0^\infty e^{-\frac{2t}{\tau}} dt = -\frac{u_0^2}{r} \cdot \frac{rC}{2} \left| e^{-\frac{2t}{\tau}} \right|_0^\infty = \frac{Cu_0^2}{2}$$

Kondensatorning zaryadsizlanishi unda to`plangan elektr energiyasi miqdoriga bog`liq

$$W_e = \frac{Cu_0^2}{2}$$

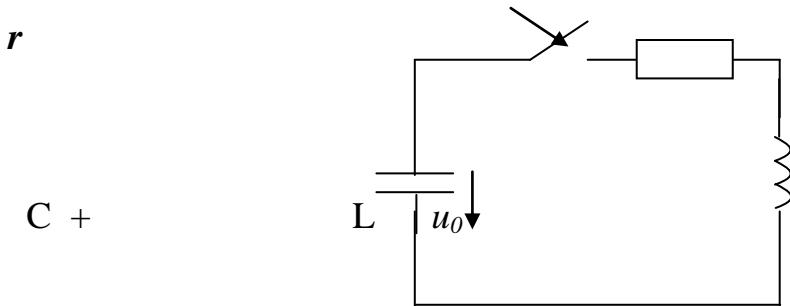

Shu. o`tkinchi jarayon tugagandan keyin tok va kuchlanishlarning turg`unlashgan qiymatlari nolga teng. Zanjirning differensial tenglamasi:

$$\frac{d^2i}{dt^2} + \frac{r}{L} \frac{di}{dt} + \frac{i}{LC} = 0 \quad (1)$$

$$\frac{r}{L} = 2\delta; \quad \omega_0^2 = \frac{1}{LC}$$

$$\alpha^2 + 2\delta\alpha + \omega_0^2 = 0 \quad (2)$$

Uning ildizlari:

$$\alpha_1 = -\delta + \sqrt{\delta^2 - \omega_0^2}$$

$$\alpha_2 = -\delta - \sqrt{\delta^2 - \omega_0^2}$$

$$i = A_1 e^{\alpha_1 t} + A_2 e^{\alpha_2 t}$$

Zanjir o`tkinchi jarayon r, L va C parametrlarning miqdorlari nisbati bilan aniqlanadi. Unda nisbat uch variantda bo`lishi mumkin:

1) α_1 va α_2 ildizlar qaqiqiy va turlich, yani $\delta^2 - \omega_0^2 > 0$;

2) α_1 va α_2 ildizlar qaqiqiy va teng, ya`ni $\delta^2 - \omega_0^2 = 0$;

3) $\delta^2 - \omega_0^2 < 0$ bo`lganda $\alpha_1 = -\delta + j\sqrt{\omega_0^2 - \delta^2}$ } ildizlar qo`shma kompleslardan
 $\alpha_2 = -\delta - j\sqrt{\omega_0^2 - \delta^2}$ } iborat.

Dastlabki ikki variantda kondensatorning zaryadsizlanishi aperiodik xarakterda bo`lib, uchinchi variantda esa bu jarayon davriy yoki tebranma bo`ladi.

Sinov savollari.

- Qisqa tutashuv qolatida g`altakdagagi magnitaviy maydon energiyasi qanday energiya turiga aylanadi?
- O`tkinchi jarayon intensivligini qanday kattalik xarakterlaydi?

3. Sig`imdagи turg`unlashgan kuchlanishni yozib bering?
4. So`nish koeffisienti α qanday aniqlanadi?