

## 32-ma`ruza. Chastota ajratuvchi elektr filtrlarni hisoblash.

Reja.

1. Quyi chastotali filtrlarni hisoblash
2. Yuqori chastotali filtrlarni hisoblash

### 1. Quyi chastotali filtrlarni hisoblash

II-simon almashtirish sxemasi bo`yicha yig`ilg`an quyi chastotali filtr  $f=0-1$  kGts diapozondagi tiniqlik zonasiga ega  $L=0.1$  Gn bo`lsa quyidagilar aniqlansin. 1) filtrning parallel tarmoqlaridagi sig`im. 2)  $f_1=1.2$  kGts chastotadagi so`nish koeffisienti. 3)  $f=0.2; 0.6; 1.2$  kGts chastotalardagi xarakteristik qarshilik.

1) Paralel tarmoqning sig`imini quyidagilardan aniqlaymiz.

$$\omega_0 = \frac{2}{\sqrt{LC}} \quad \text{dan} \quad C' = \frac{C}{2} = \frac{4}{2L\omega_0^2} = \frac{2}{0,05 [2\pi \cdot 1000]^2} = \frac{2 \cdot 10^{-9}}{0,05 \cdot 39,5} \approx 10^{-6} \text{ F}$$

2)  $f_1=1.2$  kGts chastotadagi to`rtqutblikning doimiysi.

$$A = 1 - \frac{\omega_1^2 LC}{2} = 1 - \frac{57 \cdot 10^6 \cdot 0,05 \cdot 2 \cdot 10^6}{2} = -1,85$$

$\omega \geq \omega_0$  chastotada  $\beta = \pi - \text{const}$  bo`lgani uchun  $\alpha = \frac{A}{\cos \beta}$

bo`lishiga asoslanib,  $f_1=1.2$  kGts chastotadagi so`nish koeffisientini topamiz.


$$\alpha = 1,225$$

3) Filtrning xarakteristik qarshiligi quyidagicha topiladi.

$$Z_{\text{cn}} = \sqrt{\frac{L}{C}} \cdot \frac{1}{\sqrt{1 - \frac{\omega^2}{\omega_0^2}}} = \frac{158}{\sqrt{1 - \frac{\omega^2}{\omega_0^2}}} = \frac{158}{\sqrt{1 - \left(\frac{f}{f_0}\right)^2}}$$


$f=0.2; 0.6; 1.2$  kGts chastotalardagi xarakteristik qarshiliklar
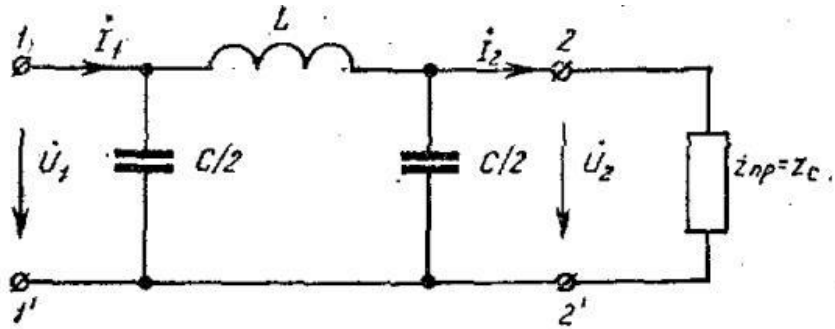
$$Z_{\text{cn}_1} = \frac{158}{\sqrt{1 - 0,2^2}} = \frac{158}{0,98} = 161 \text{ Om}, \quad Z_{\text{cn}_2} = \frac{158}{\sqrt{1 - 0,6^2}} = \frac{158}{0,8} = 198 \text{ Om},$$
$$Z_{\text{cn}_3} = \frac{158}{\sqrt{1 - 1,2^2}} = \frac{158}{j 0,663} = -j 238 \text{ Om}.$$


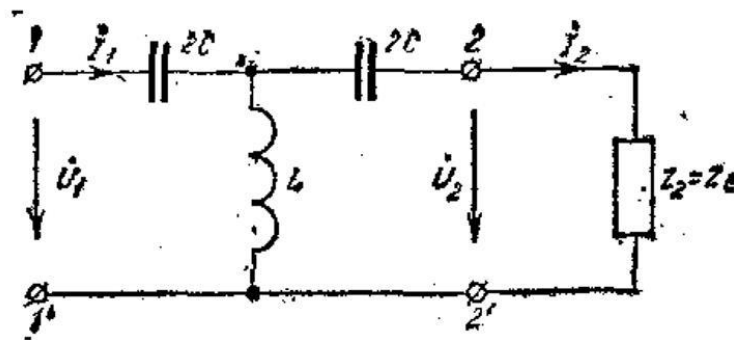
## 2. Yuqori chastotali filtrlarni hisoblash

T-simon yuqori chastotali filtrning parametrlari  $C=1 \text{ mk F}$  va  $L=0.01 \text{ Gn}$ . Quyidagilar aniqlansin. 1) filtrning tiniqlik zonasini hosil qiluvchi chastotalar diapozoni. 2)  $\omega = 0.8 \omega_0$  chastotadagi so`nish koeffisienti. 3) faza koeffisienti va filtrning  $\omega = 2 \omega_0$  chastotadagi xarakteristik qarshiligi.



1) Filtrning o`tkazish chastotasi

$$\omega_0 = \frac{1}{2\sqrt{LC}} = \frac{1}{2\sqrt{10^{-6} \cdot 10^{-2}}} = \frac{10^4}{2} = 5 \cdot 10^3 \text{ rad/sek}$$

$$f_0 = \frac{\omega_0}{2\pi} = 797 \text{ Гц} \approx 800 \text{ Гц}$$

$5 \omega_0^3 - \infty$  Demak filtrning tiniqlik zonasi diapozonda bo`ladi.

2)  $\omega = 0.8 \omega_0$  chastotadagi so`nish koeffisienti. Dastlab filtrning shu chastotadagi parametric A ni to`rtqutblikka o`xshash aniqlaymiz

$$A = 1 - \frac{2\omega_0^2}{\omega^3} = 1 - \frac{2}{0.64} = 1 - 3.13 = -2.13$$

chastotada faza koeffisienti  $0 < \omega < \omega_0$  bo'lganligidan

$$\operatorname{ch} \alpha = \frac{A}{\cos \beta} = \frac{-2,13}{-1} = 2,13, \quad \alpha = 1,39$$

3)  $\omega = 2 \omega_0$  chastotadagi faza koeffisienti

$$\cos \beta = 1 - 2 \cdot \frac{1}{2^2} = 0,5 \quad \beta = \frac{\pi}{3} \text{ рад.}$$

$\omega = 2 \omega_0$  chastotadagi xarakteristik qarshilik

$$\begin{aligned} Z_{\text{ex}} &= \sqrt{\frac{B}{C}} = \sqrt{\frac{Z_1 + Z_2 + Z_1 \cdot Z_2 \cdot Y_0}{Y_0}} = \sqrt{\frac{L}{C} - \frac{1}{4\omega^2 C^2}} = \sqrt{\frac{3L}{4C}} \\ &= \sqrt{\frac{3 \cdot 10^{-2}}{4 \cdot 10^{-6}}} = 0,866 \cdot 10^2 = 86,6 \text{ Ом} \end{aligned}$$

### Sinov savollari.

1. Chastota ajratuvchi filtrlar deb nimaga aytiladi?
2. Quyi chatota filtrlarining ishlash prinsipini tushintiring?